

NEC芯片原理图一用78K0/78K0S来控制DC传动器

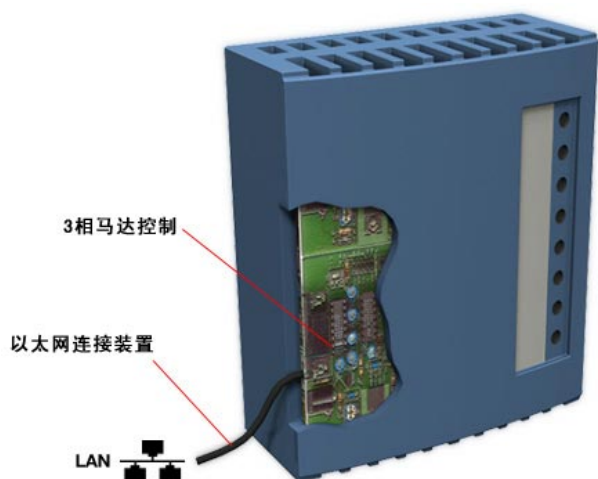


图 (1)

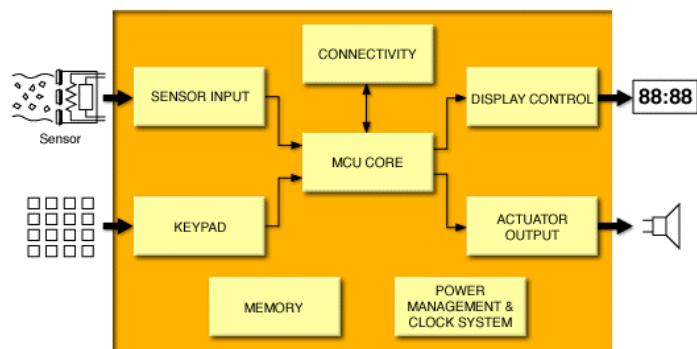


图 (2)

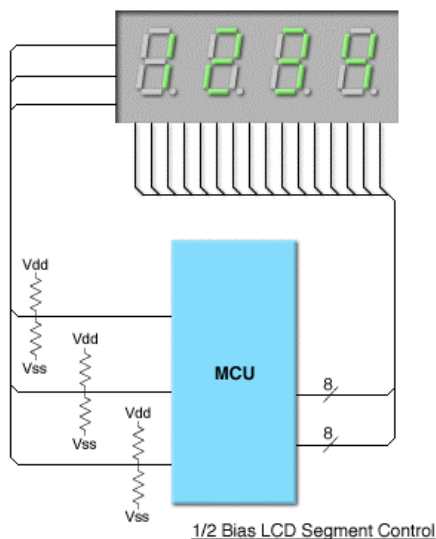


图 (3)

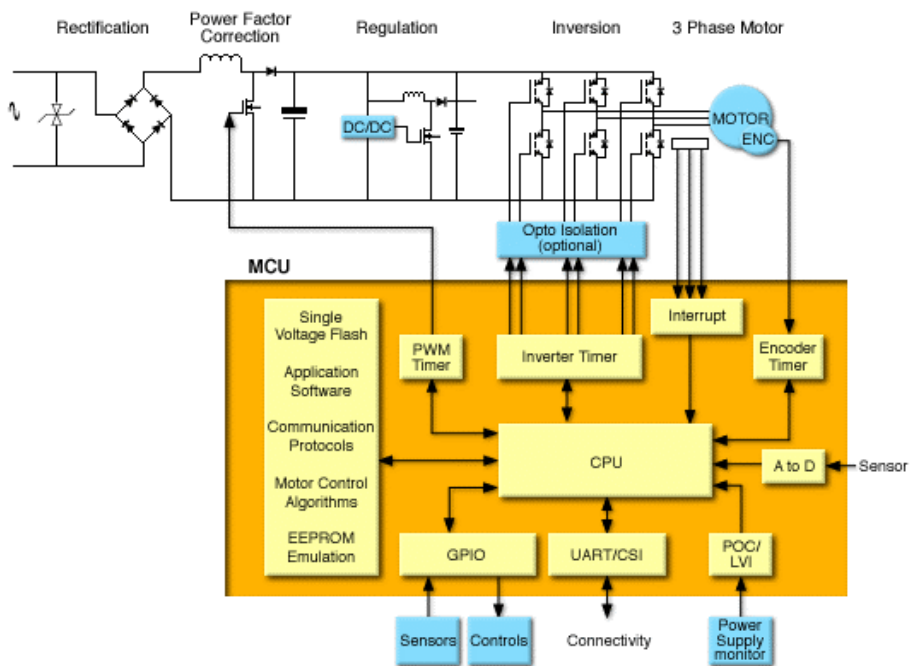


图 (4)